

### 3-)Boost Converter (Webench)

First of all, I chose,  $V_{in,min}=4.8\text{ V}$ ,  $V_{in,max}=5.2\text{ V}$ , output 12 V at 2 A and 25 °C. I sorted all of the results. Finally, I select TPS61088 because it has highest efficiency with 95.8 and low BOM area with 123 mm<sup>2</sup>. Its cost is average. BOM cost of it is \$3.53 and IC cost of it is \$1.60.

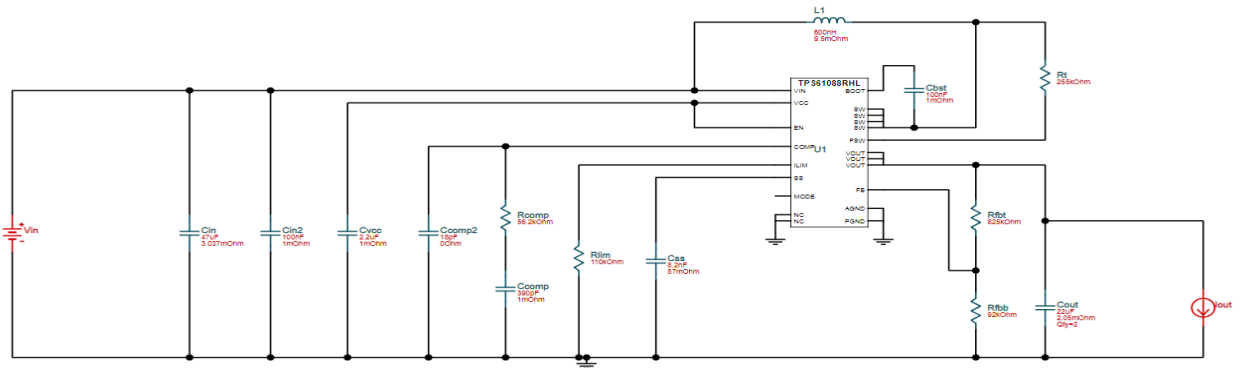


Figure 1: Circuit Schematic of TPS61088 (Boost converter)

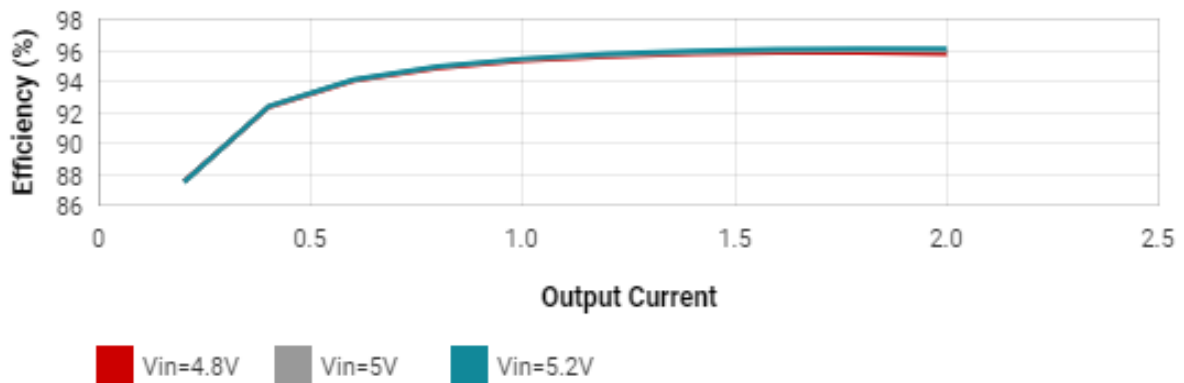


Figure 2: Efficiency vs Output current graph of TPS61088

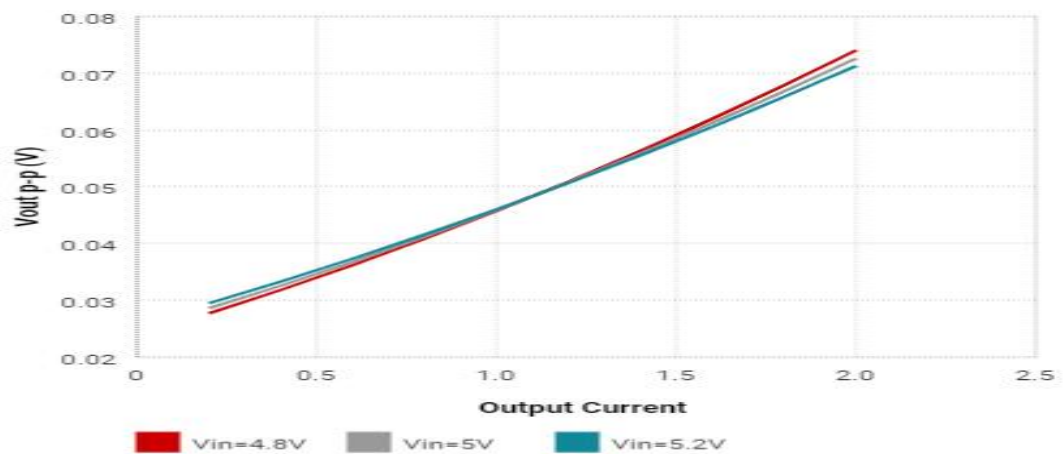



Figure 3: Output voltage ripple vs Output current graph of TPS61088

**Table 1 : Operation Values of TPS61088**


Inductor Current Peak to Peak Value	8.2 A
Output Voltage Peak to Peak Value	74.05 mV
Efficiency	%95.8
IC Junction Temperature	53.33 °C
Mode	BOOST CCM
FootPrint	123 mm <sup>2</sup>
BOM Cost	\$3.53

**Table 2: Power Dissipation of circuit elements of TPS61088**


Cin	17.04 mW
Cout	8.73 mW
L	301.54 mW
IC	730.06 mW
Total	1.06 W

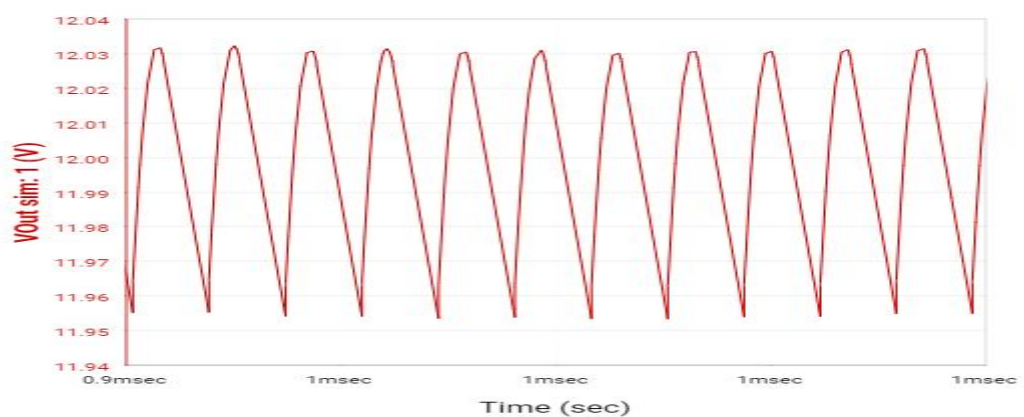

**Figure 4: Output Voltage vs Time Graph for Steady-State of TPS61088**

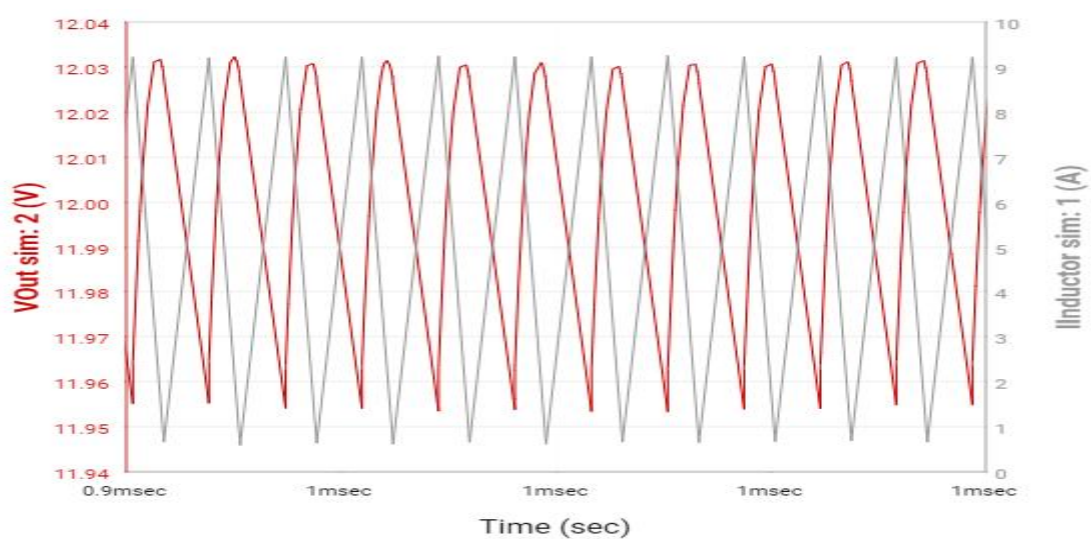

**Figure 5: Inductor Current vs Time Graph for Steady-State of TPS61088**

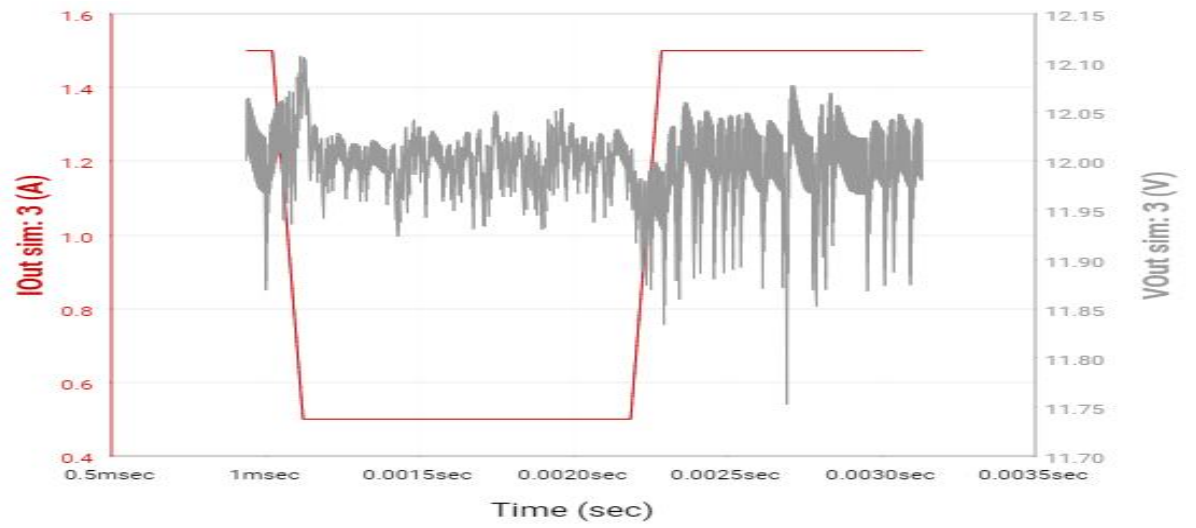

**Figure 6: Output Voltage & Load Current vs Time for Load Transient of TPS61088**